
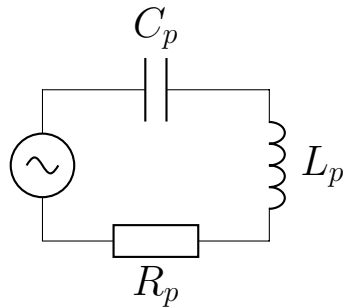


Seminar - 9th week

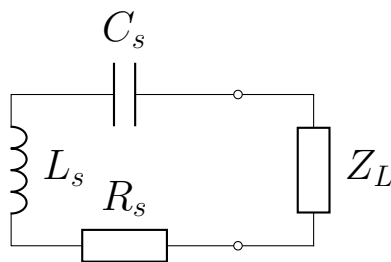1. The Power Transmitter of the Qi wireless charger can be modeled by the simplified model according to the circuit diagram:




- The inductance is $L_p = 25 \mu\text{H}$ and resonant frequency $f_p = 100 \text{ kHz}$. The Quality factor of the circuit is $Q = 100$. Calculate values of capacitance C_p and resistance R_p .
2. At start-up, the voltage source in the Qi Power Transmitter from previous task has the voltage $v_{ping} = 24 \text{ V}$ with frequency $f_{ping} = 175 \text{ kHz}$. Calculate voltage on inductor v_L . Calculate voltage on inductor v_L , which would be at resonant frequency $f_p = 100 \text{ kHz}$ assuming the Transmitter is not coupled with Receiver. Calculate the current in the circuit in such a case (note that the current limit is 3 A).
 3. The Power Receiver of the Qi wireless charger can be modeled by the simplified model according to the circuit diagram:



The inductance is $L_s = 35 \mu\text{H}$ and resonant frequency $f_s = 100 \text{ kHz}$. The Quality factor of the circuit (without load impedance Z_L) is $Q_s =$

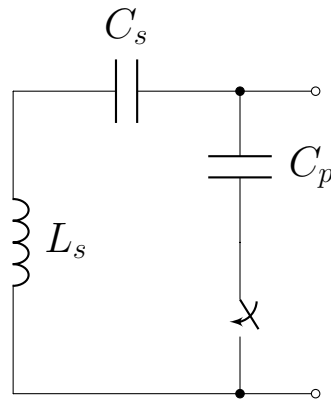
40. Calculate values of capacitance C_s and resistance R_s .

In the detection phase is in the Receiver connected parallel capacitor C_p , according to the figure below.



The parallel resonant frequency is $f_d = 1 \text{ MHz}$. Calculate capacitance of capacitor C_p .

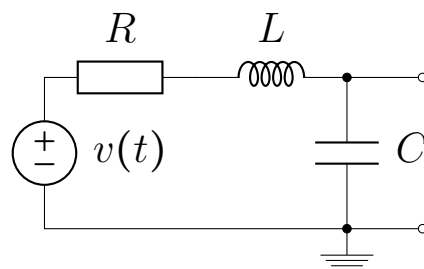4. The circuit below is supplied from sinusoidal voltage source $v(t) = 1 \sin \omega t$. The inductance $L = 10 \text{ mH}$ and resistance $R = 1 \Omega$. Angular frequency $\omega = 10\,000 \text{ rad s}^{-1}$. The circuit is in the resonance. Calculate:
- Capacitance C
 - Magnitude of capacitor voltage V_C
 - Draw magnitude frequency response (Bode plot) for the capacitor voltage.



5. Parallel RLC resonant circuit is supplied by the sinusoidal current source with magnitude 10 mA . $C = 1 \mu\text{F}$, $L = 0.1 \text{ H}$, $R = 10 \Omega$.
- Calculate resonant frequency.
 - Calculate impedance of the circuit in resonance, source voltage and current in capacitor.

c) What is the quality factor of the circuit?

