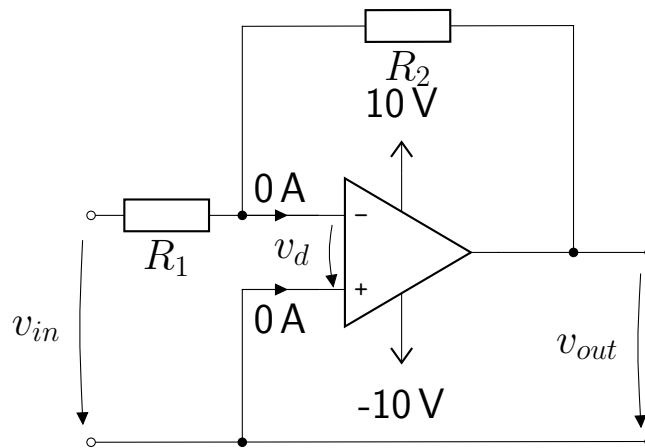



# Seminars - 3<sup>rd</sup> week

1. The kettle has an input power of 1000 W. To heat up 1 liter of water from 20 °C to 100 °C lasts for 7 minutes. What is kettle energy efficiency?
2. DC current 1 mA flows in the capacitor with capacitance 100 nF.
  - a) Compute the charge stored in the capacitor at  $t = 1$  ms.
  - b) Compute the voltage across capacitor's terminals at  $t = 1$  ms.
  - c) Determine the energy stored in the capacitor at  $t = 1$  ms.
  - d) Draw waveforms of charge, voltage and stored energy for DC current source, as well as for triangular, rectangular and sinusoidal waveforms of source current).
3. Find voltage across capacitor with capacitance 45  $\mu$ F, if it stores energy 400 J.
4. The inductor with inductance  $L = 2$  H is connected to DC voltage source  $V = 12$  V. The initial current was zero.
  - a) Compute the current in the inductor at  $t = 2$  s.
  - b) Determine the energy stored in the inductor at  $t = 2$  s.
  - c) Is possible just simply disconnect inductor from the voltage source?
5. The resistive load is connected to the MOSFET switch with wire which has inductance  $L = 50$   $\mu$ H. The current falls from the value  $I = 10$  A to zero within time interval of  $t = 1$   $\mu$ s. Calculate voltage on the MOSFET transistor.
6. The circuit in the figure below contains an ideal operational amplifier. It can be replaced with voltage-controlled voltage source. It has two inputs,  $v_+$  and  $v_-$ , input resistance is infinite, and the gain  $A \rightarrow \infty$ , so, for finite output voltage  $v_{out}$  the input differential voltage  $v_d = V_+ - v_- \rightarrow 0$ .  
Find general relation between  $v_{in}$  and  $v_{out}$ . Find  $v_{out}$ , if  $R_1 = 100$  k $\Omega$ ,  $R_2 = 10$  k $\Omega$  and  $v_{in} = 0.1$  V.



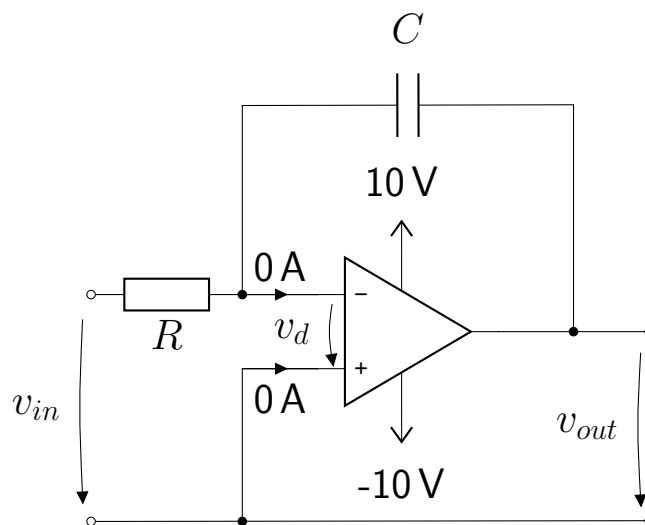
7. The circuit in the figure below contains an ideal operational amplifier.

- Find general relation between  $v_{in}$  and  $v_{out}$ .
- Find values of  $R$  and  $C$ , if the input voltage is rectangular waveform with magnitude  $\pm 1\text{ V}$  and period  $2\mu\text{s}$ , the output voltage should be triangular waveform with amplitude of  $5\text{ V}$ .



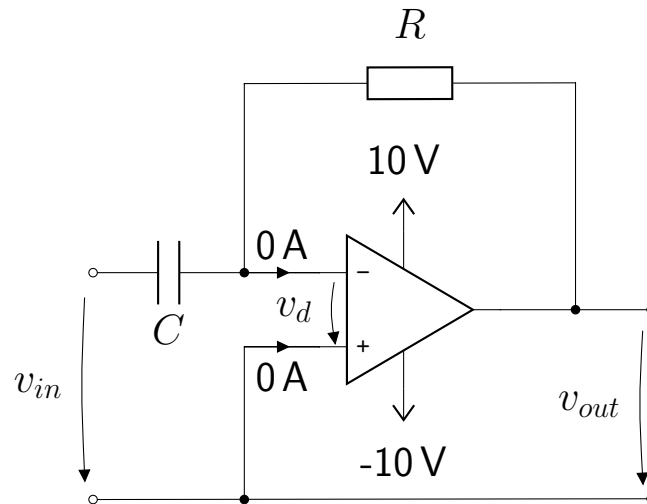8. The circuit in the figure below contains an ideal operational amplifier.

- Find general relation between  $v_{in}$  and  $v_{out}$ .
- Find values of  $R$  and  $C$ , if the input voltage is triangular waveform with magnitude  $\pm 1\text{ V}$  and period  $2\mu\text{s}$ , the output voltage should have amplitude of  $5\text{ V}$ .



9. In the network in the figure below find

- Currents  $I_1$ ,  $I_2$  and  $I_3$ .
- All voltages, and resistance  $R_1$ , if  $R_2 = 600\ \Omega$ ,  $R_3 = 1\ \text{k}\Omega$ ,  $R_4 = 6\ \text{k}\Omega$ ,  $R_5 = 1\ \text{k}\Omega$ .

