

Excitation by single pulses, unit impulse and unit step response.

Pavel Máša



EXAMPLE

To the input of the circuit, we connected voltage source of the waveform

$$u_1(t) = 10e^{i 500t} \text{ V}$$

On the output, we measured the waveform



$$u_2(t) = 6.6(e^{i 500t} - e^{i 2000t}) \text{ V}$$

Find transfer function of the circuit. Find suitable circuit diagram.



$$U_1(p) = \frac{10}{p + 500}$$

$$U_2(p) = \frac{6.6}{p + 500} - \frac{6.6}{p + 2000} = \frac{6.6 \cdot 2000 - 6.6 \cdot 500}{(p + 500)(p + 2000)} = \frac{10000}{(p + 500)(p + 2000)}$$
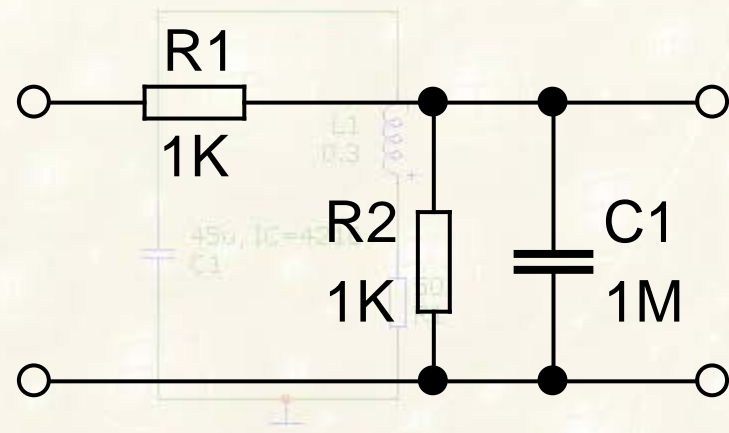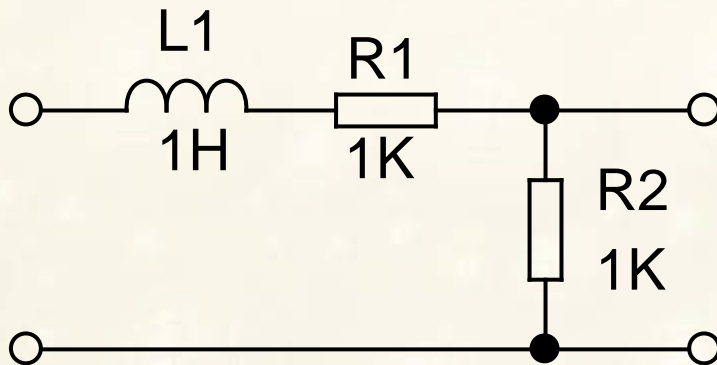
$$P(p) = \frac{U_2(p)}{U_1(p)} = \frac{\frac{10000}{(p + 500)(p + 2000)}}{\frac{10}{p + 500}} = \frac{1000}{p + 2000}$$



EXAMPLE

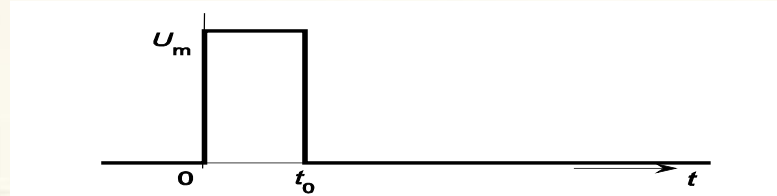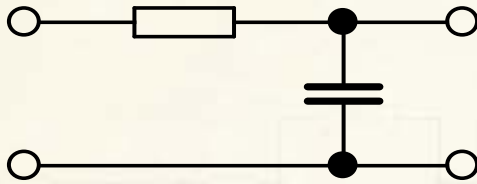


The integrating network in the figure is excited by rectangular pulse in second figure. Compute the waveform of output voltage. **The capacitor has zero voltage at the time of connection of source (zero initial condition).**

- To find the solution we will use table of Laplace transforms
- rectangular pulse is superposition of two unit step functions multiplied by U_m

$$1. \quad U_1(p) = \frac{U_m}{p} [1 - e^{-pt_0}]$$

$$2. \quad P(p) = \frac{1}{1 + pRC}$$
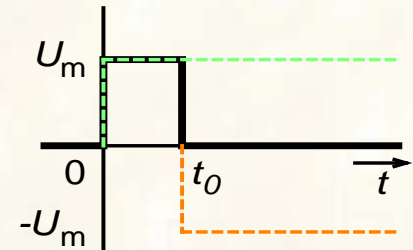
$$3. \quad U_2(p) = U_1(p) \cdot P(p) = \frac{U_m}{p} \frac{1}{1 + pRC} \cdot 1 \cdot e^{-pt_0}$$




Statement in the square bracket will be temporary omitted (it is information about time delay, transformed later)

$$U_2'(p) = \frac{A}{p} + \frac{B}{p + \frac{1}{RC}} = U_m \left(\frac{1}{p} - \frac{1}{p + \frac{1}{RC}} \right) \Rightarrow u_2'(t) = U_m \left(1 - e^{-\frac{t}{RC}} \right)$$


The transform of the square bracket are two unit step functions, the second is time shifted by t_0


$$u_2(t) = U_m \left[(1 - e^{-\frac{t}{RC}})1(t) - (1 - e^{-\frac{t-t_0}{RC}})1(t - t_0) \right]$$

EXCITATION BY THE UNIT STEP FUNCTION

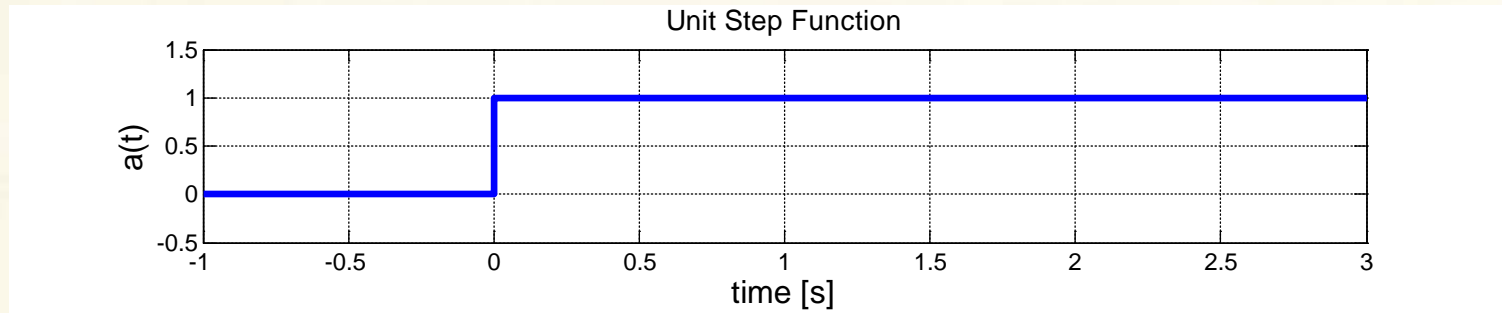

- Consider linear circuit, with zero energetic initial conditions.
- Unit step response is an output of a such circuit, if it is excited by the Unit step function.
- In time domain, it give us important information about rise time, overshoot, settling time.
- In frequency domain, we got information about frequency response of the circuit, and we can calculate response on any excitation.
- In frequency domain, we can assess stability of the circuit.

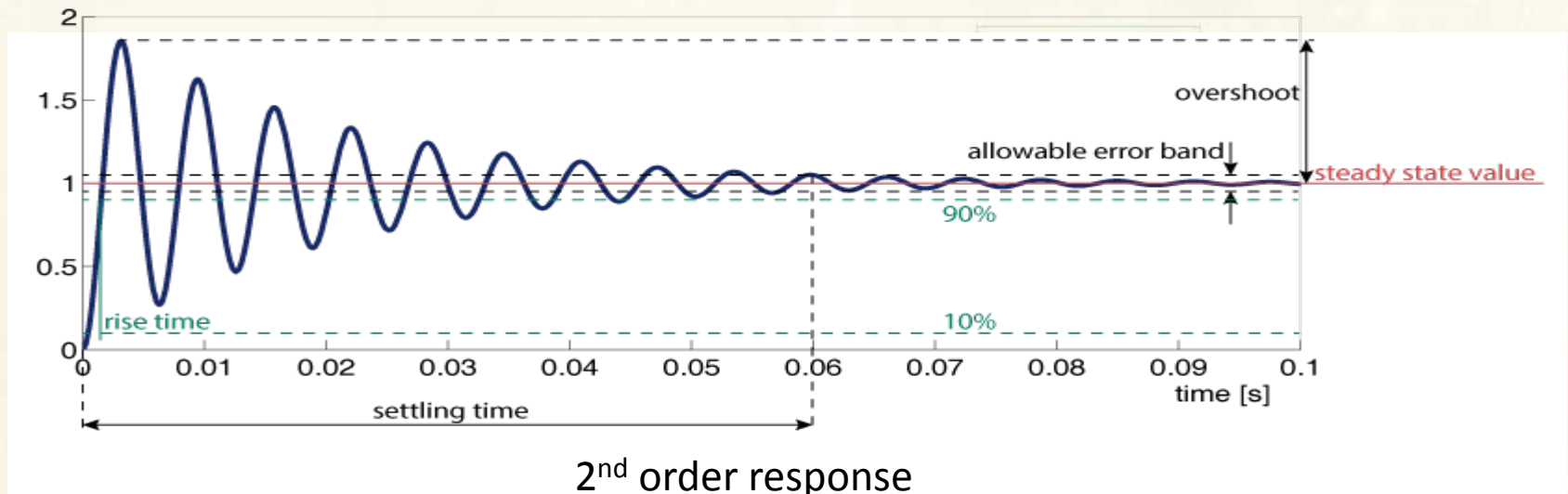

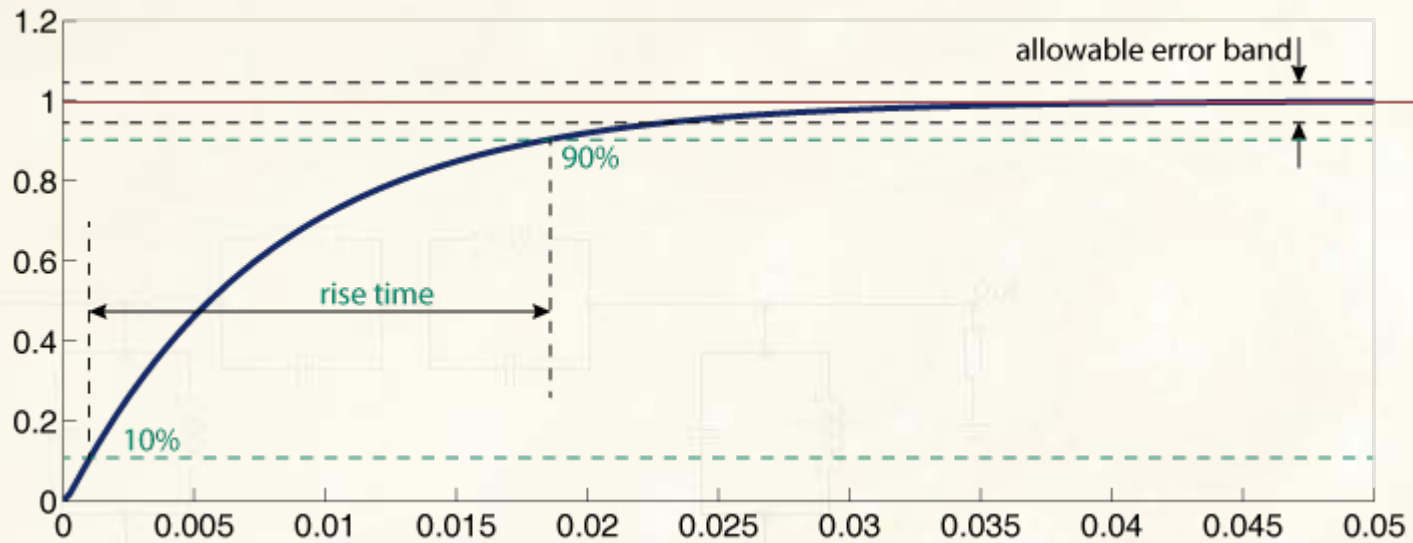

1st order response

Input – unit step function

$$u_1(t) = a(t)$$



Output – unit step response $H(t) = u_2(t)$

Using Laplace transform:

$$A(p) = \frac{1}{p} H(p) \quad \text{where } H(p) \text{ is the transfer function}$$



EXCITATION BY THE UNIT IMPULSE FUNCTION

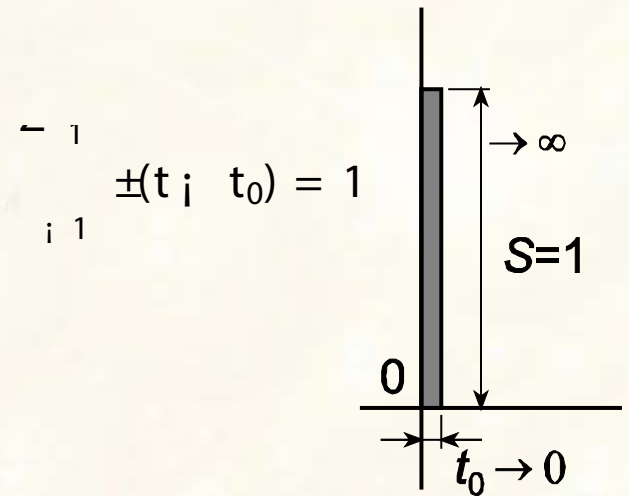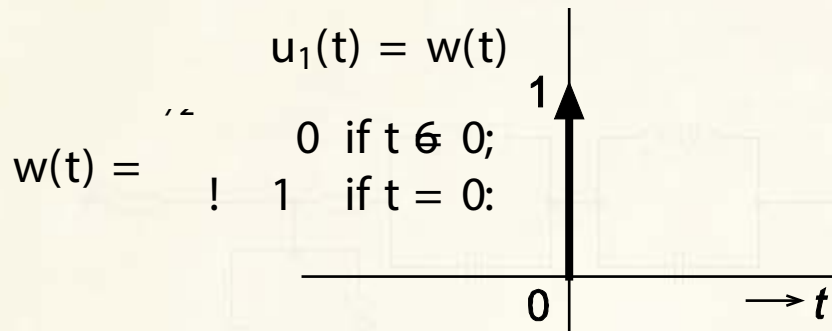

- Consider linear circuit, with zero energetic initial conditions.
- Unit impulse response is an output of a such circuit, if it is excited by the Unit impulse function.
- It give us information about transfer function.
- Connect unit impulse source to the input, measure output response, convert it to Laplace domain, and we get the transfer function


$$W(p) = H(p) = \int_0^\infty u_2(t) g$$

$$w(t) = \frac{da(t)}{dt} \quad a(t) = \int_0^t w(t) dt$$



Periodical rectangular waveform – integrating circuit

τ

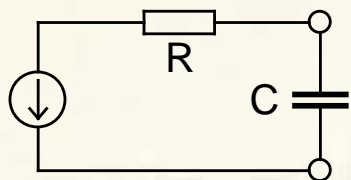

$$\tau = 1 \text{ ms}$$

$$R = 1 \text{ k}\Omega; C = 1 \text{ }^1 \text{ F}$$

$$U_m = 1 \text{ V}$$

$$T = 20 \text{ ms} \rightarrow \tau_0 = 100\%$$

Periodical steady state:

$$u_1(t) = 0.5 + \sum_{k=1}^{\infty} \frac{2}{(2k-1)^{1/4}} \sin(2k-1)\omega_0 t \quad U_{01} = 0.5, \hat{U}_{1k} = \frac{2}{(2k-1)^{1/4}}$$

$$U_{02} = 0.5, \hat{U}_{2k} = \hat{U}_{1k} \frac{1}{1 + j(2k-1)\omega_0 RC} = \frac{2}{(2k-1)^{1/4}} \frac{1}{1 + j(2k-1)0.1}$$

$$u_2(t) = 0.5 + 0.607 \sin(314.16t - 0.304) + 0.154 \sin(942.48t - 0.756) + 0.068 \sin(1570.79t - 1.004) + \dots$$

Transient:

$$t \in (0; 0.1) \quad u_2(t) = 1 - e^{-1000t}$$

$$u_2(0.01) = 0.9999546 \text{ V}$$



$$t \in (0.1; 0.2) \quad u_2(t) = 0.9999546 e^{-1000(t-0.1)}$$

$$u_2(0.02) = 0.0000454 \text{ V}$$


$$t \in (0.2; 0.3) \quad u_2(t) = 1 - 0.9999546 e^{-1000(t-0.2)}$$

In this case each change of excitation voltage will be considered as the origin of new transient

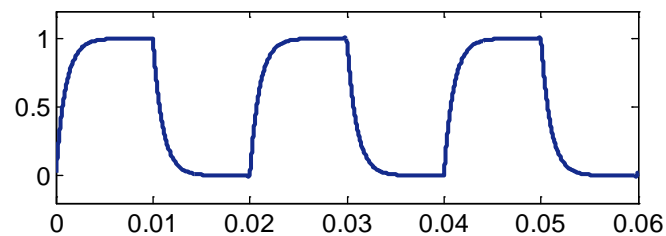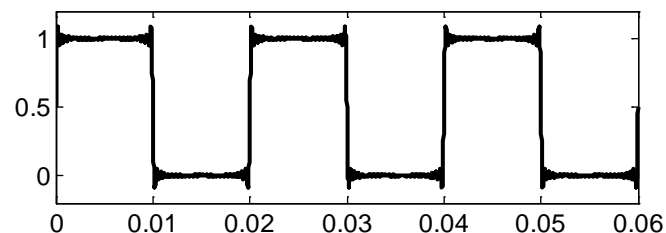– the *transient voltage* at the end of first half of the period is the *initial condition* of subsequent transient
in this case may be omitted




i Δ T

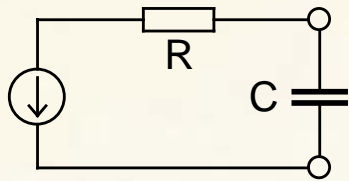



$$i = 1 \text{ ms}$$

$$R = 1 \text{ k}\Omega; C = 1 \text{ }^1 \text{ F}$$
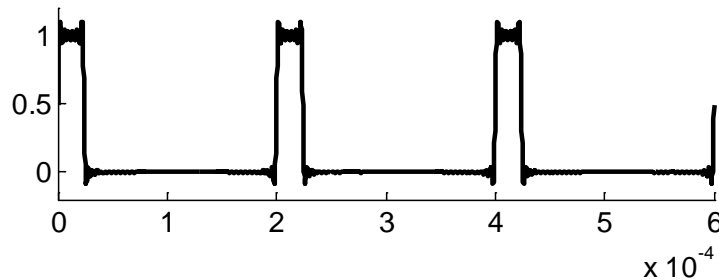
$$T = 0.2 \text{ ms} \rightarrow !_0 = 10000\%$$



Periodical steady state:

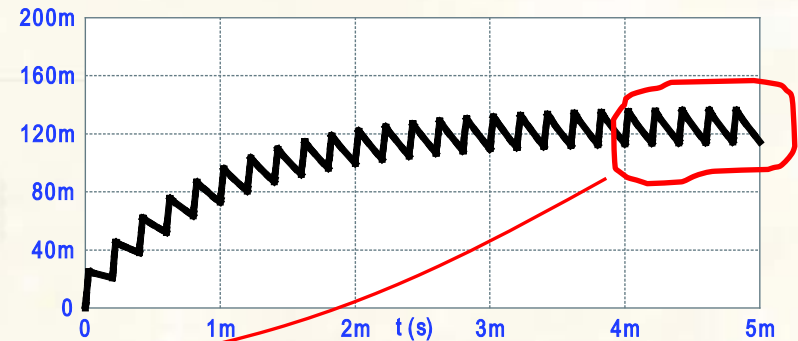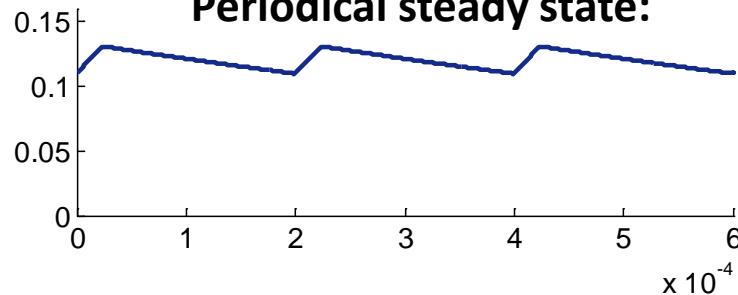

Periodical steady state does not resolve transient part, but just steady state part – it is equal to the **mean value** of rectangular waveform

Exponential trend is equivalent to the „slow“ transient with time constant τ

$$u_1(t) = \sum_{k=i-1}^{\infty} \hat{U}_{1k} e^{j k \omega t} \quad U_{01} = \frac{U_m \zeta t_0}{T} = 0.12, \quad \hat{U}_{1k} = \frac{U_m}{j k 2^{1/4}} e^{j k \omega t_0} i^{-1} = \frac{1}{j k 2^{1/4}} e^{j k 0.24^{1/4}} i^{-1}$$

$$U_{02} = U_{01}, \quad \hat{U}_{2k} = \hat{U}_{1k} \frac{1}{1 + j k \omega_0 R C} = \frac{1}{j k 2^{1/4}} e^{j k 0.24^{1/4}} i^{-1} \zeta \frac{1}{1 + j k 10^{1/4}} \quad k = i-1; ::; i-1; 1; ::; 1$$

$$t \in (0; 24^1 \text{ s}) \quad u_2(t) = 1 - e^{-1000t}$$

$$t \in (24^1 \text{ s}; 200^1 \text{ s}) \quad u_2(t) = 0.0237143 e^{-1000(t - 0.000024)}$$

$$t \in (200^1 \text{ s}; 224^1 \text{ s}) \quad u_2(t) = 1 - 0.9801127 e^{-1000(t - 0.0002)}$$


...

$$u_2(24^1 \text{ s}) = 0.0237143 \text{ V}$$

$$u_2(200^1 \text{ s}) = 0.01988723 \text{ V}$$

$$u_2(224^1 \text{ s}) = 0.04312991 \text{ V}$$

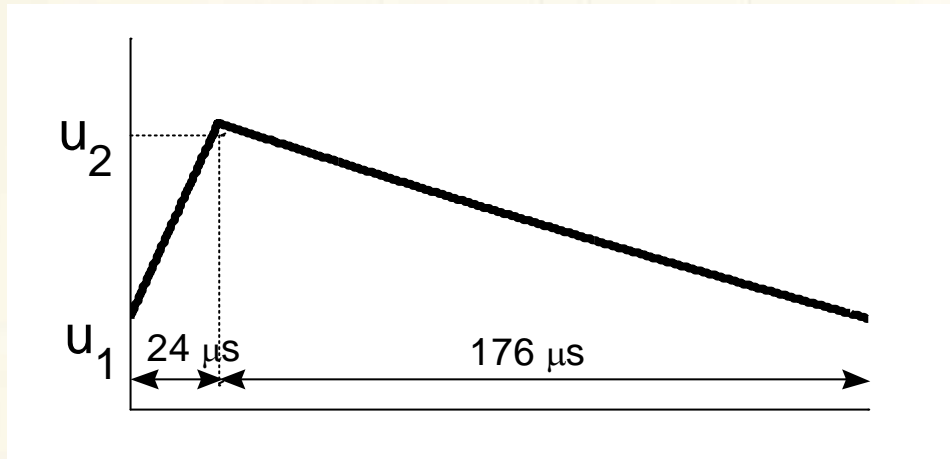Steady state – how from the transient equation find limit voltages:



1st part – increasing exponential

$$u_c(0) = u_1; \quad u_p = 1; \quad t = 24^1 \text{ s}$$

$$u(24^1 \text{ s}) = u_2 = (u_1 - 1) e^{-0.024} + 1$$

2nd part – decreasing exponential

$$u_c(0) = u_2; \quad u_p = 0; \quad t = 176^1 \text{ s}$$

$$u(176^1 \text{ s}) = u_1 = u_2 e^{-0.176}$$





Set of equations

$$\begin{cases} 1 - e^{-0.024} - u_1 = 0 \\ u_1 - e^{-0.176} u_2 = 0 \end{cases}$$

$$u_1 = 0.109711$$



$$u_2 = 0.130824$$

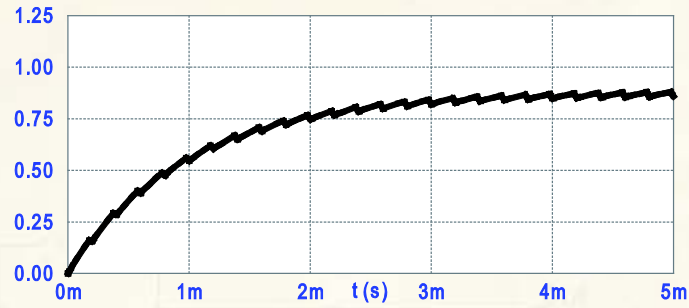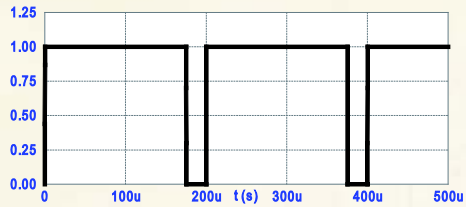

Positive mean value

$$U_{\max} = 1$$



$$U_{\min} = 0$$

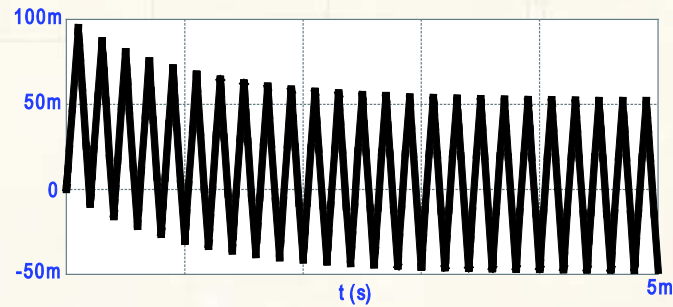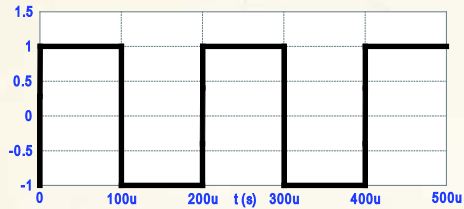

Zero mean value

$$U_{\max} = 1$$



$$U_{\min} = -1$$

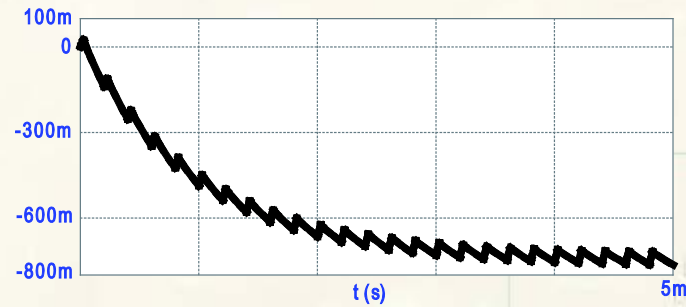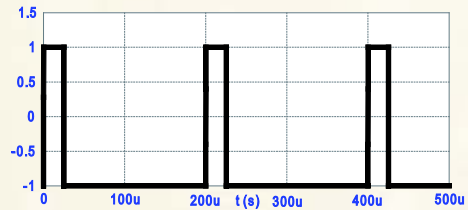

Negative mean value

$$U_{\max} = 1$$

$$U_{\min} = -1$$

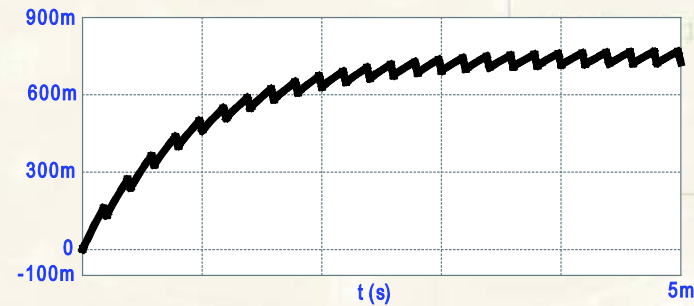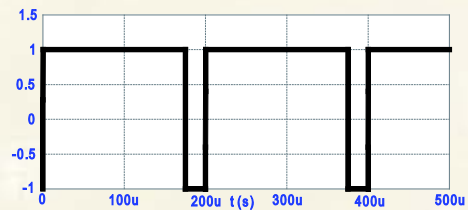


Positive mean value

$$U_{\max} = 1$$

$$U_{\min} = -1$$

Periodical rectangular waveform – derivative circuit

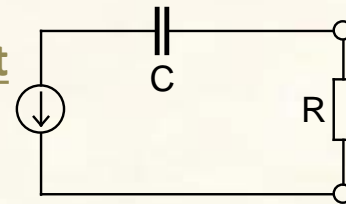
RC circuit exhibits „derivative“ properties, only when $\tau \ll T$



$$R = 1 \text{ k}\Omega; C = 1 \mu\text{F}$$

$$\tau = 1 \text{ ms}$$

$$U_m = 1 \text{ V}$$

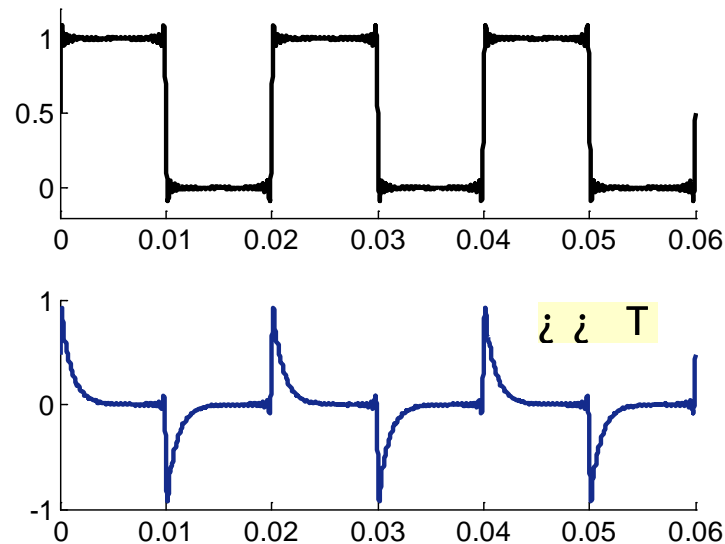

$$T = 20 \text{ ms} \rightarrow f_0 = 100 \text{ Hz}$$


$$u_1(t) = 0.5 + \sum_{k=1}^{\infty} \frac{2}{(2k-1)^{1/4}} \sin(2k-1)\pi f_0 t$$

$$U_{01} = 0.5, U_{1k} = \frac{2}{(2k-1)^{1/4}}$$

$$U_{02} = 0$$

$$U_{2k} = U_{1k} \frac{j(2k-1)\pi f_0 RC}{1 + j(2k-1)\pi f_0 RC}$$
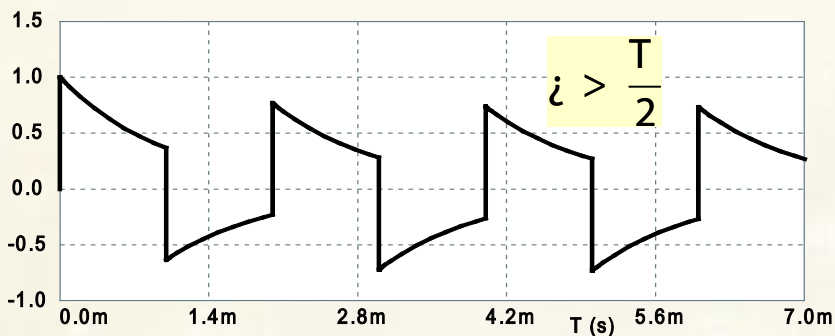
$$= \frac{2}{(2k-1)^{1/4}} \frac{j(2k-1)\pi f_0 RC}{1 + j(2k-1)\pi f_0 RC}$$



$$u_c(t) = [u_c(0) + u_{cp}(0)] e^{-\frac{t}{\tau}} + u_{cp}(t)$$

$$i(t) = C \frac{du_c(t)}{dt} = \frac{C}{R} [u_c(0) + u_{cp}(0)] e^{-\frac{t}{\tau}}$$

$$u_2(t) = Ri(t) = \frac{RC}{\tau} [u_c(0) + u_{cp}(0)] e^{-\frac{t}{\tau}}$$


$$= [u_{cp}(0) + u_c(0)] e^{-\frac{t}{\tau}} = u_R(0) e^{-\frac{t}{\tau}}$$

$u_{cp}(0)$ is particular solution on capacitor – alternatively 1 V (first half period) and 0V

$u_R(0)$ positive on rising edge, negative on falling edge $u_R(0)_n = \pm 1 - u_R(\frac{T}{2})_{n-1}$

i Δ T Derivative circuit
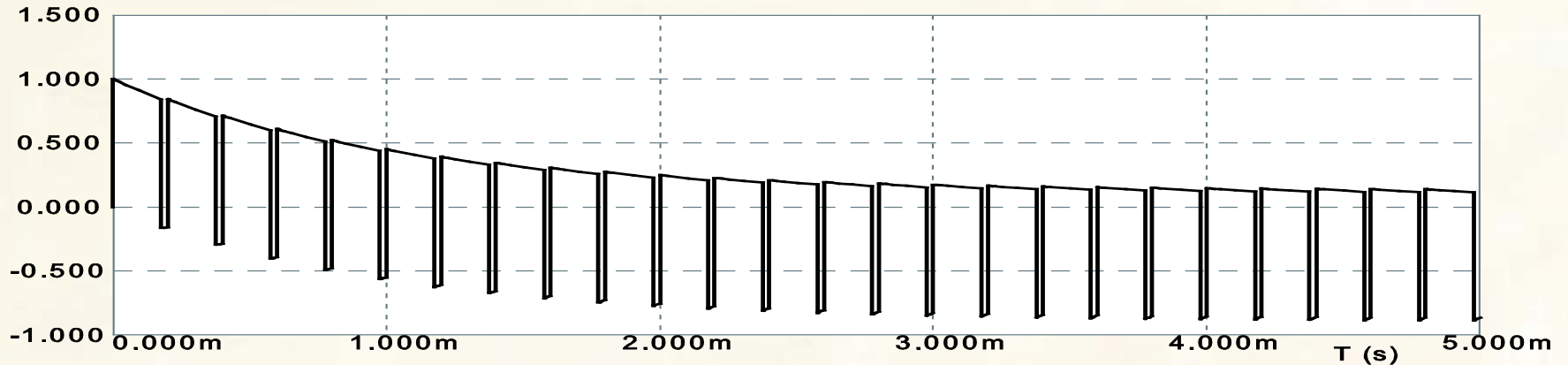
$$i = 1 \text{ ms} \quad T = 0.2 \text{ ms} \quad t_0 = 176 \text{ }^1 \text{ s}$$



- The voltage is almost rectangular, if the duration of voltage values are: U_m is t_0 and 0 is $T - t_0$, than the waveform has boundary voltages $U_m \frac{t_0}{T}$ and $U_m (1 - \frac{t_0}{T})$
- The magnitude is still U_m
- „Slow“ exponential transient is boundary waveform
- The waveform of the voltage across capacitor is the same as voltage across capacitor in the integrating circuit above (the sum of both voltages must be in each time instant U_m).

