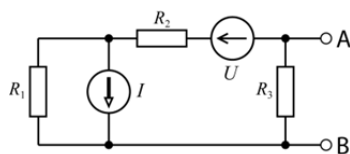


# Fundamentals of electrical circuits – sample exam test

## 1) DC I (10 marks)


- For the circuit in the figure calculate voltage  $U_{AB}$  between the terminals A, B.
- From the viewpoint of terminals A, B draw the Thévenin's (or Norton's) equivalent circuit.
- Calculate parameters of this equivalent circuit.

$U = 80 \text{ V}$ ,  $I = 6 \text{ mA}$ ,  $R_1 = 5 \text{ k}\Omega$ ,  $R_2 = 1 \text{ k}\Omega$ ,  $R_3 = 4 \text{ k}\Omega$ .


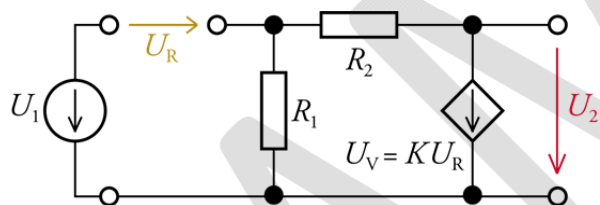
## 2) DC II (10 marks)


Circuit in the figure contains voltage controlled voltage source. Calculate voltage  $U_2$ , if  $U_1 = 0.5 \text{ V}$ ,  $R_1 = 1 \text{ k}\Omega$ ,  $R_2 = 4 \text{ k}\Omega$ ,  $K = 20000 [-]$ ,  $U_V = K U_R$ .



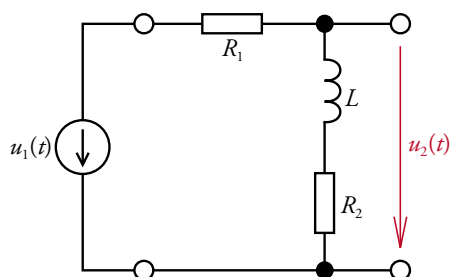3) Frequency response (10 marks)


For circuit in the figure draw magnitude and phase frequency response (Bode plot) of the voltage transfer function

$$\mathbf{P} = \frac{U_2}{U_1}. R_1 = 18 \text{ k}\Omega, R_2 = 2 \text{ k}\Omega, L = 0.4 \text{ H}.$$



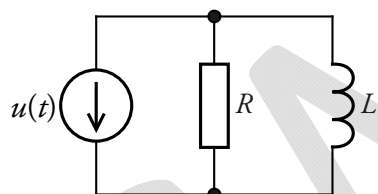4) AC power (10 marks)

For the circuit in the figure calculate active, reactive and apparent power, drawn from the voltage source  $u(t) = 100 \sin(5000t) \text{ V}$ ,  $R = 500 \Omega$ ,  $L = 100 \text{ mH}$ .




5) Resonant circuit. (10 marks)

Series RLC circuit (see figure) is supplied from sinusoidal voltage source with amplitude 1V.

$C = 1\mu\text{F}$ .

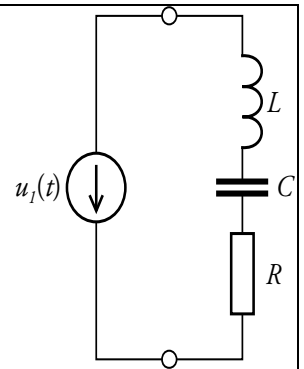- Calculate inductance of the inductor, if the resonant frequency is  $\omega_r = 1000 \text{ rad s}^{-1}$ .
- Calculate the resistivity of resistor, if the amplitude of voltage across capacitor terminals in steady state in resonance is 100 V.
- Find total current, which flows in the circuit.




6) 1<sup>st</sup> order transients (10 marks)

Circuit in the figure was at  $t < 0$  in a steady state (the switcher  $P$  was in the right-handed position at this time). At  $t = 0$  the switcher „P“ was switched to the left-handed position. Calculate both the waveform of the current  $i_L(t)$  passing the inductor, and the voltage  $u_x(t)$ .

$U = 120 \text{ V}$ ,  $I = 30 \text{ mA}$ ,

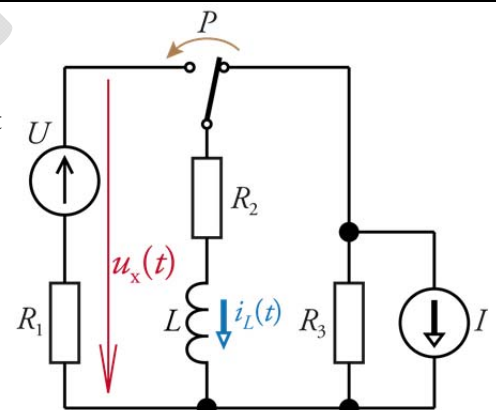$R_1 = 200 \Omega$ ,  $R_2 = 400 \Omega$ ,  $R_3 = 800 \Omega$ ,  $L = 24 \text{ mH}$ .



7) 2<sup>nd</sup> order circuit (10 marks)

RLC circuit in the figure was in a steady state at  $t < 0$ . The switcher “S” was off at this time, and the capacitor was charged to the voltage  $u_C(0) = 4000$  V. **At time  $t = 0$  the switcher „S“ was switched on.**  
 $R = 50\ \Omega$ ,  $L = 0.3$  H,  $C = 45\ \mu\text{F}$ .

- Write circuit equation, which describes current in the circuit.  
*You can write this equation in the time domain (integral-differential equation), or using Laplace transform, whatever you prefer.*
- Calculate roots of the equation from step a.  
*(characteristic equation – time domain, or polynomial in denominator – Laplace transform).*
- Write a general solution of electrical current waveform in the circuit (general solution of the transient). **Don't calculate** integration constants, or, don't perform partial fraction decomposition (in the case of Laplace transform solution).

