

Seminar - 10th week - results

1. a) $S = 0.000\,01 + 0.01j$ VA, $P = 10\,\mu\text{W}$, $Q = 10\,\text{mvar}$, $S = 10.1\,\text{mVA}$.
 b) $S = 10 + 0.000\,715j$ VA, $P = 10\,\text{W}$, $Q = 715\,\mu\text{var}$, $S = 10\,\text{VA}$.
2. $P = 2.5\,\text{W}$, $Q = -25\,\text{var}$, $S = 25.1247\,\text{VA}$.
3. The load is inductive, the angle is $0.7954\,\text{rad}$, or 45.573° (and $S = 14\,286\,\text{VA}$, $Q = 10\,202\,\text{var}$).
4. $I = 208.33\,\text{A}$, and power loss in the line is $P = 4.34\,\text{kW}$. After pf compensation current falls on $I = 131.58\,\text{A}$ and power loss is just $P = 1.73\,\text{kW}$.
5. a) $S = 105.83 + 105.83j$, $P = 105.83\,\text{W}$, $Q = 105.83\,\text{var}$.
 b) $Z = 500.14 + 500.14j$. $R = 500.14\,\Omega$, $L = 1.592\,\text{H}$.
 c) $P_R = 21.16\,\text{W}$, $Q_L = 6.65\,\text{var}$.
 d) $S = 169.64\,\text{VA}$.
6. $V = 262.46 - 12.075j = 262.73/\underline{-0.046}$.