

DC - Combining resistors

Total resistance:

- a) $R = 2.\overline{3} \text{ k}\Omega$
- b) $R = 4.4 \text{ k}\Omega$
- c) From the left handed side $R = 1550 \Omega$, right handed side $R = 1950 \Omega$
- d) $R = 2 \text{ k}\Omega$
- e) It is necessary to use tranfiguration, $R = 2094.\overline{594} \Omega$

Special values of circuit variables (average and rms values)

1) 1:3 $U_s = \frac{1}{4}U_m = 3 \text{ V}, U = U_m\sqrt{\frac{1}{4}} = 6 \text{ V}$

3:1 $U_s = \frac{3}{4}U_m = 9 \text{ V}, U = U_m\sqrt{\frac{3}{4}} = 10.39 \text{ V}$

2) $U_m = 325.27 \text{ V}$

Sinusoidal waveform: $U_{sar} = \frac{2U_m}{\pi} = 207.07 \text{ V}$

Full way rectified: $U = 230 \text{ V}, U_s = U_{sar} = 207.07 \text{ V}$

Half way rectified: $U = \frac{U_m}{2} = 162.635 \text{ V}, U_{sar} = \frac{U_m}{\pi} = 103.535 \text{ V}$

3) $U = 208.05 \text{ V}$

Fundamental passive and active circuit elements

1. $C = 8 \text{ F}$.

- a. $V = 1600 \text{ cm}^3$.
- b. $t = 16 \text{ s}$.
- c. Current.

2. $U = 4216 \text{ V}$.

- a. $V = 377 \text{ cm}^3$.
- b. Price.

3.

- a. $Q = 1 \cdot 10^{-6} \text{ C}$
- b. $U = 10 \text{ V}$
- c. $W_C = 5 \cdot 10^{-6} \text{ J}$
- d. Waveforms have equations $q(t) = It + q(0) = 10^{-3}t \text{ [C]}, u(t) = \frac{q(t)}{C} = 10^4 t \text{ [V]},$
 $W_C(t) = \frac{1}{2}Cu^2(t) = \frac{1}{2C}q^2(t) = 5t^2 \text{ [J]}.$

4. $I = 2.4 \text{ A}$

5. $U = -R \cdot I = -200 \cdot 2.4 = -480 \text{ V}$

6.

- a. $C = 8 \mu\text{F}$
- b. $U_1 = 160 \text{ V}, U_2 = 40 \text{ V}.$
- c. $U_1 = 36.36 \text{ V}, U_2 = 54.54 \text{ V}, U_3 = 109.09 \text{ V}.$
- d. At $t \rightarrow \infty$ will be the same. At $t = 0$ the voltage on capacitors is zero, and capacitors will be gradually charged.
- e. $Q = 1.6 \text{ mC}.$
- f. $U_1 = 40 + 124 = 164 \text{ V}, U_2 = 5 + 31 = 36 \text{ V}.$

7.

- a. $L = 8 \text{ mH}.$
- b. $I_1 = 1.6 \text{ A}, I_2 = 0.4 \text{ A}.$


Basic laws and theorems, simple circuits excited by one and several independent sources

1.

- a. $I = 0.123 \text{ A}.$
- b. $U_{R_1} = 22.154 \text{ V}, U_{R_2} = 1.846 \text{ V}$
- c. $P_{R_1} = 2.736 \text{ W}$ - power rating at least 3 W, ceramic or metal oxide resistor, $P_{R_2} = 0.23 \text{ W}$ - power rating at least 250 mW, metal film or carbon film resistor, $P = 2.954 \text{ W}$

2.

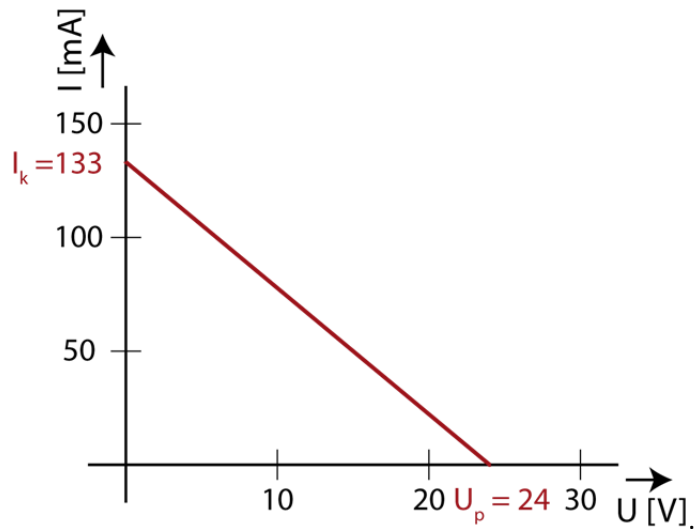- a. $U_{R_2} = 1.154 \text{ V}.$
- b. $U_2 = 0 \text{ V}, I = 0.133 \text{ A}.$



- c.
- d. $U_i = U_{R_2} = 1.846 \text{ V}, R_i = 13.88 \Omega.$
- e. $I_z = 0.00667 \text{ A}.$

3. Arrangement 2 / 2.

- a) $R_p = 7.14 \Omega, P_z = 16.8 \text{ W}.$
- b) $P_R = 7 \text{ W}.$

4.

- a. $U = 1.11 \text{ V}.$

- b. No, the source with higher voltage discharges in the source with lower voltage, part of energy converts in heat
- c. $I_1 = 6 \text{ A}, I_2 = 4 \text{ A}, I = 10 \text{ A}.$
- d. $U_i = 1.11 \text{ V}, R_i = 0.11 \Omega.$
- e. $I_{max} = 1 \text{ A}.$

5.

- a. Yes.


6.

- a. No.
- b. $U_v = 9.375 \text{ V}.$
- c. $I = 110 \text{ A}.$

7.

- a. $I = 0.39 \text{ A}.$
- b. $P_{U_1} = 1.95 \text{ W}, P_{U_2} = -0.429 \text{ W}, P_{R_1} = 1.521 \text{ W}$

8. Yes,

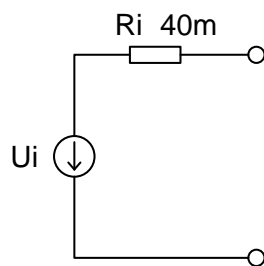

$U_i = 12 \text{ V}.$ Load line has parameters $U_i = 12 \text{ V}$ and $I_k = 300 \text{ A}.$

- 9. No, it acts like ideal current source.
- 10. No, it acts like ideal voltage source.

Kirchhoff's laws

1)

- a) $I_1 = 10 \text{ mA}, I_2 = 15 \text{ mA}, I_4 = 20 \text{ mA}$
- b) $R_1 = 900 \Omega, R_2 = 400 \Omega, R_4 = 150 \Omega, V_2 = 6 \text{ V}$
- c) $P_U = 300 \text{ mW}, P_I = -30 \text{ mW}$

2)

- a) $I_1 = 5 \text{ mA}, I_2 = 10 \text{ mA}, I_3 = 0 \text{ mA}, I_4 = 5 \text{ mA}$
- b) $U_2 = 5 \text{ V}, R_2 = 700 \Omega$

3)

- a) $I_B = 4.37 \mu\text{A}$
- b) $U_x = -8.91 \text{ V}$

4)

- a) $U_x = 9 \text{ V}$
- b) $U_T = 9 \text{ V}, R_T = 3 \text{ k}\Omega$

5) $U_x = 10.929 \text{ V}$

Source transformation

- 1) $U_T = 5.6 \text{ V}, R_T = 0.8 \Omega$
- 2) $U_x = -2.05 \text{ V}$

Circuit Theorems and Basic Laws

- 1)
 - a) $U_d = 2.86 \text{ mV}$
 - b) $R_{load} = 349.997 \Omega, U_d = 1.43 \text{ mV}$. Maximum power transfer condition maximizes power transfer, however, the output voltage is twice less, which has no meaning for voltage measuring. Contrarily, less voltage may cause less accuracy.
- 2) $U_x = 6 \text{ V}$
- 3) $U_x = 18 \text{ V}$
- 4) $U_x = 24.6 \text{ V}$
- 5) $U_x = 60.968 \text{ V}$
- 6) $U_x = 68.71 \text{ V}$
- 7) $I_{U_1} = 30 \text{ mA}, I_{U_2} = 25 \text{ mA}, U_x = 0 \text{ V}$
- 8)
 - a) $U_{R_1} = 0 \text{ V}, U_{R_2} = 0 \text{ V}, U_{R_3} = 20 \text{ V}, U_{R_4} = -80 \text{ V}$
 - b) $P_U = 0 \text{ W}, P_I = 20 \text{ W}, P_R = 4 + 16 = 20 \text{ W}$

Circuit equations

- 1) $I_x = -24.\overline{4} \text{ mA}$
- 2) $I_x = 2.5 \text{ mA}$
- 3) $U_x = -30.\overline{30} \text{ mV}$