
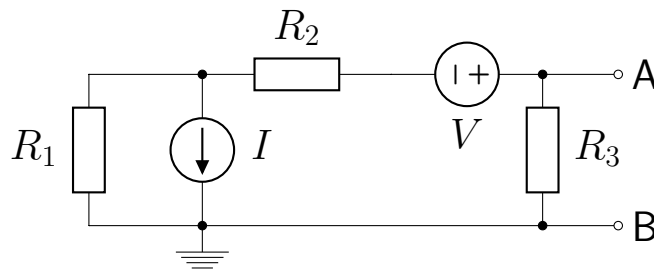


Seminars - 5th week

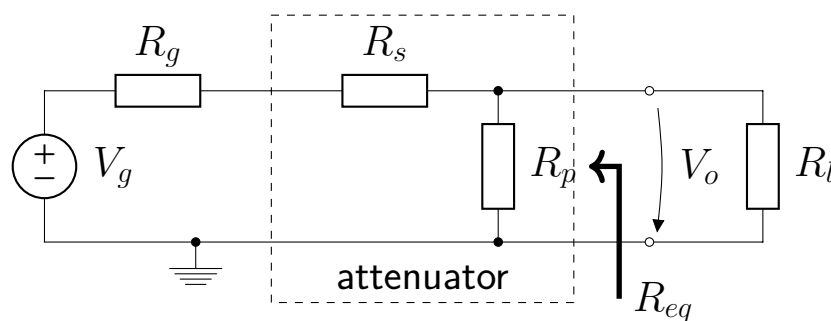
1. For the circuit in the figure below find its Thevenin equivalent circuit seen at terminals A-B. $V = 16\text{ V}$, $I = 32\text{ mA}$, $R_1 = 1\text{ k}\Omega$, $R_2 = 4\text{ k}\Omega$, $R_3 = 3\text{ k}\Omega$.



2. An attenuator is an interface circuit that reduces the voltage level without changing the output resistance (it is important, if we connect e.g. coaxial cable to the output of generator).
 - a) Find values of R_s and R_p to meet the following requirements: $\frac{V_o}{V_g} = 0.125$ and $R_{eq} = R_g = 100\ \Omega$.
 - b) Using the attenuator designed in previous step find current through a load of $R_l = 50\ \Omega$, if $V_g = 24\text{ V}$.



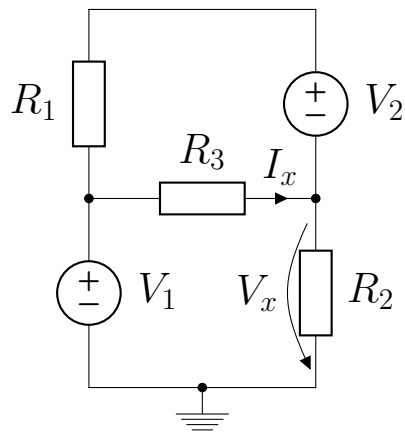3. For the circuit in the figure calculate voltage V_x and current I_x . $V_1 = 40\text{ V}$, $V_2 = 32\text{ V}$, $R_1 = 2\text{ k}\Omega$, $R_2 = 3\text{ k}\Omega$, $R_3 = 2\text{ k}\Omega$.



4. For the circuit in the figure calculate voltage V_x and current I_x . $V = 50\text{ V}$, $I = 10\text{ mA}$, $R_1 = 1\text{ k}\Omega$, $R_2 = 2\text{ k}\Omega$, $R_3 = 3\text{ k}\Omega$.

