
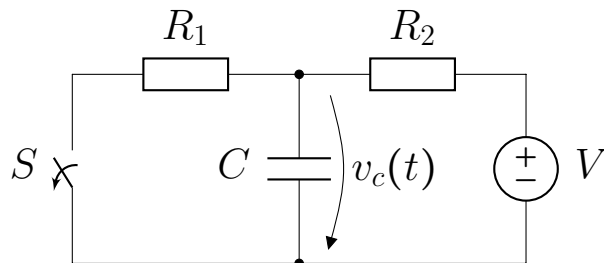


Seminar - 11th week

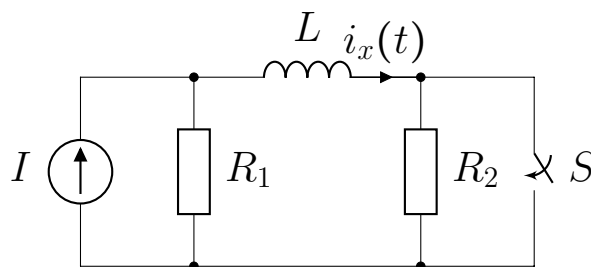
1. The switch in the circuit has been closed for a long time, and it is opened at $t = 0$. Calculate $v_c(t)$ for $t \geq 0$. Draw its waveform both at $t < 0$ and $t \geq 0$. $V = 18\text{ V}$, $R_1 = 1.2\text{ k}\Omega$, $R_2 = 3.6\text{ k}\Omega$, $C = 3\text{ }\mu\text{F}$.




2. The switch in the circuit has been opened for a long time, and it is closed at $t = 0$. Calculate $i_x(t)$ for $t \geq 0$. Draw its waveform both at $t < 0$ and $t \geq 0$. $I = 0.8\text{ A}$, $R_1 = 180\text{ }\Omega$, $R_2 = 270\text{ }\Omega$, $L = 7.2\text{ mH}$.



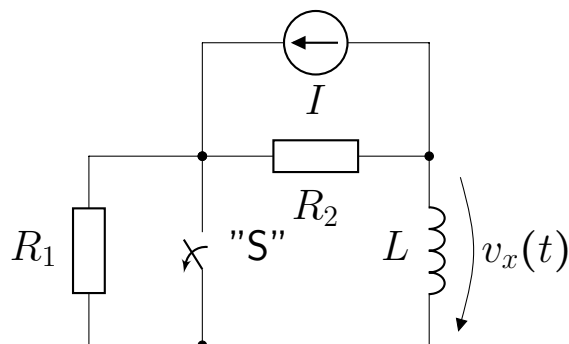
3. The switch in the circuit has been closed for a long time, and it is opened at $t = 0$. Calculate $v_x(t)$ for $t \geq 0$. Draw its waveform both at $t < 0$ and $t \geq 0$. $I = 25\text{ mA}$, $R_1 = 820\text{ }\Omega$, $R_2 = 180\text{ }\Omega$, $L = 0.25\text{ H}$.



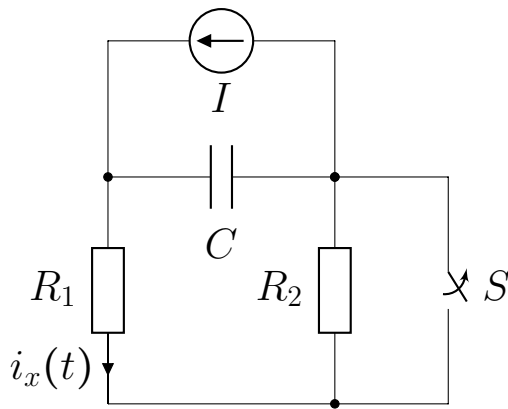
4. The switch in the circuit has been closed for a long time, and it is opened at $t = 0$. Calculate $i_x(t)$ for $t \geq 0$. Draw its waveform both at $t < 0$ and $t \geq 0$. $I = 22\text{ mA}$, $R_1 = 400\text{ }\Omega$, $R_2 = 600\text{ }\Omega$, $C = 20\text{ }\mu\text{F}$.



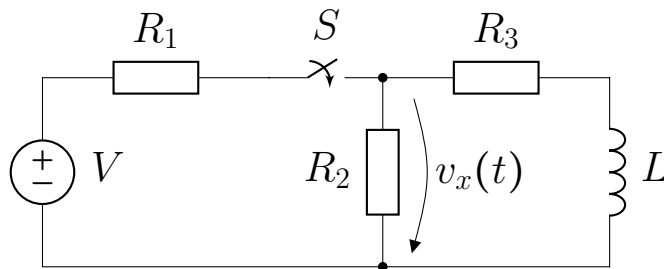
5. The switch in the circuit has been opened for a long time, and it is closed at $t = 0$. Calculate $v_x(t)$ for $t \geq 0$. Draw its waveform both at $t < 0$ and $t \geq 0$. $V = 50\text{ V}$, $R_1 = 2\text{ k}\Omega$, $R_2 = 3\text{ k}\Omega$, $R_3 = 800\text{ }\Omega$, $L = 10\text{ mH}$.



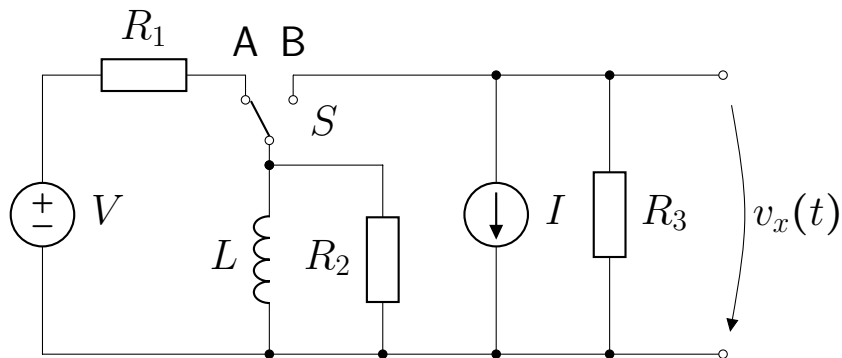
6. The switch in the circuit has been in the position A for a long time. At time $t = 0$ the switch was switched in position B. Calculate $v_x(t)$ for $t \geq 0$. Draw its waveform both at $t < 0$ and $t \geq 0$. $V = 12\text{ V}$, $I = 50\text{ mA}$, $R_1 = 1.2\text{ k}\Omega$, $R_2 = 20\text{ k}\Omega$, $R_3 = 30\text{ k}\Omega$, $L = 0.3\text{ H}$.



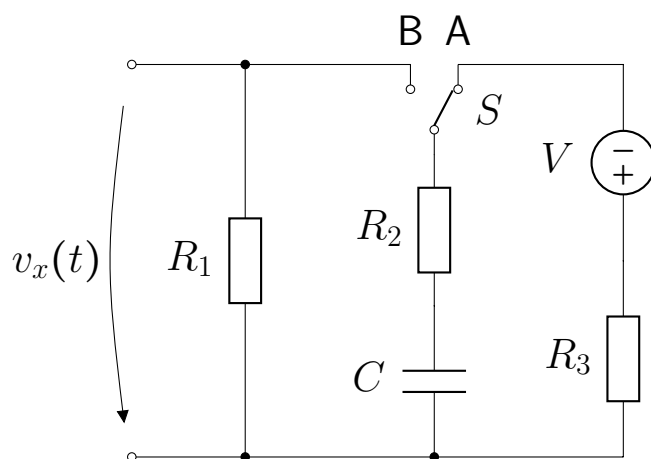
7. The switch in the circuit has been in the position A for a long time. At time $t = 0$ the switch was switched in position B. Calculate $v_x(t)$ for $t \geq 0$. Draw its waveform both at $t < 0$ and $t \geq 0$. $V = 20\text{ V}$, $R_1 = 6\text{ k}\Omega$, $R_2 = 4\text{ k}\Omega$, $R_3 = 2\text{ k}\Omega$, $C = 2\text{ }\mu\text{F}$.



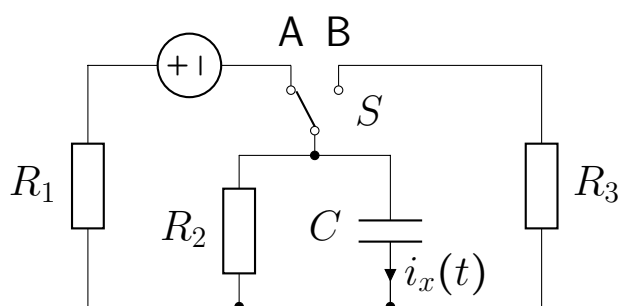8. The switch in the circuit has been in the position A for a long time. At time $t = 0$ the switch was switched in position B. Calculate current $i_x(t)$ for $t \geq 0$. Draw its waveform both at $t < 0$ and $t \geq 0$. $V = 30\text{ V}$, $R_1 = 4\text{ k}\Omega$, $R_2 = 2\text{ k}\Omega$, $R_3 = 8\text{ k}\Omega$, $C = 1\text{ }\mu\text{F}$.




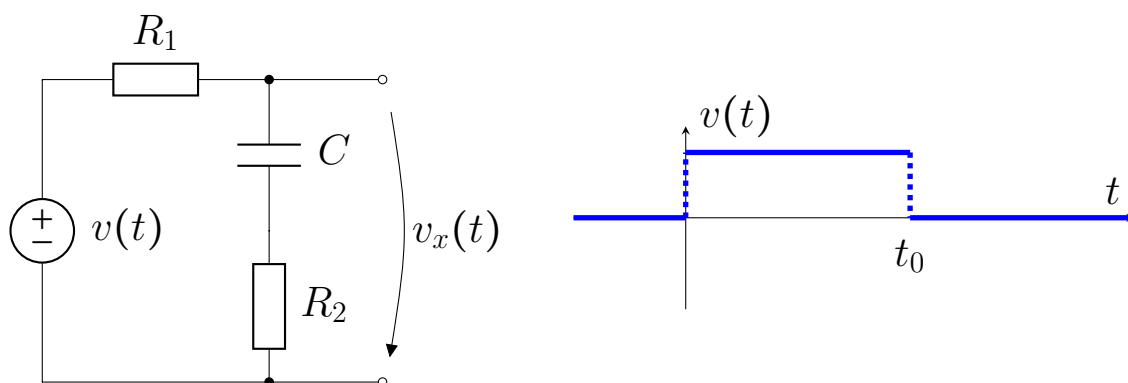9. The circuit is supplied by the voltage source, which generates single rectangular pulse according to the figure. The pulse duration is $t_0 = 10\text{ ms}$, magnitude $V = 10\text{ V}$. Calculate voltage $v_x(t)$ for $t \geq 0$. Draw its waveform both at $t < 0$ and $t \geq 0$. $R_1 = 3\text{ k}\Omega$, $R_2 = 2\text{ k}\Omega$, $C = 2\text{ }\mu\text{F}$.




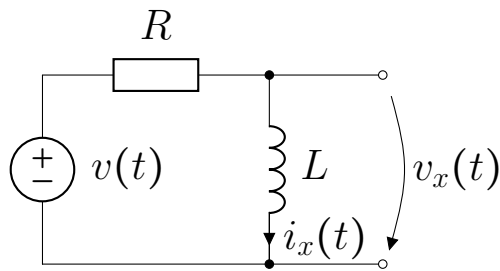10. The circuit is supplied by the voltage source, which generates periodical rectangular waveform with frequency $f = 100\text{ kHz}$. Duty cycle is $D =$

75 %. Calculate current $i_x(t)$ and voltage $v_x(t)$ within the first period. Draw their waveforms. $V = 10\text{ V}$, $R = 1\text{ k}\Omega$, $L = 0.1\text{ H}$. Simulate in Microcap waveforms of current and voltage both on inductor and resistor. Try to calculate mean value of current.



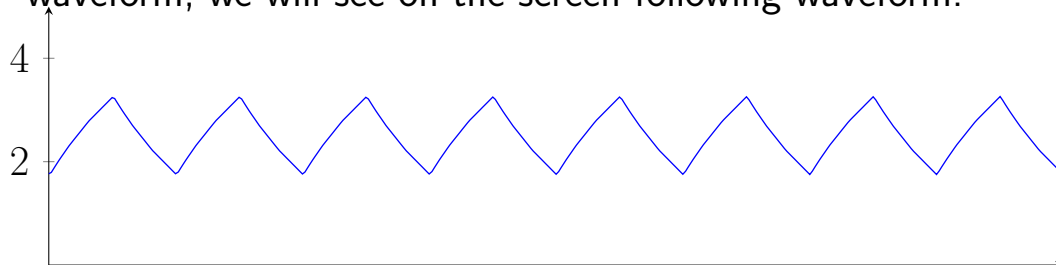11. Derivative RC circuit with time constant $\tau = 0.2\text{ ms}$ ($R = 10\text{ k}\Omega$, $C = 20\text{ nF}$) is supplied from the pulse voltage source (periodical rectangular waveform). The pulse has the magnitude of 5 V , period $T = 5\text{ }\mu\text{s}$ and duty cycle $D = 20\%$. Simulate in MicroCap a transient within the time interval $t \in (0, 200)\text{ }\mu\text{s}$ and $t \in (950, 1000)\text{ }\mu\text{s}$. Explain why the waveform is shifted above horizontal axis in the second case.
12. An integrating RC circuit with time constant $\tau = 0.2\text{ ms}$ ($R = 10\text{ k}\Omega$, $C = 20\text{ nF}$) is supplied from the pulse voltage source (periodical rectangular waveform). The pulse has the magnitude of 5 V , period $T = 5\text{ }\mu\text{s}$ and duty cycle $D = 20\%$. Simulate in MicroCap a transient within the time interval $t \in (0, 200)\text{ }\mu\text{s}$ and $t \in (950, 1000)\text{ }\mu\text{s}$. Explain why the waveform is shifted above horizontal axis in the second case.
13. During of development of a microprocessor circuit we need to check, whether the clock oscillator is running. On the output of the oscillator should be rectangular waveform with magnitude $V = 5\text{ V}$ and duty cycle $D = 50\%$. To measure the voltage, we connect an oscilloscope probe to the output of the oscillator. However, instead of rectangular waveform, we will see on the screen following waveform:



What can cause wrong shape of voltage waveform? Propose steps to find reason of the problem.