
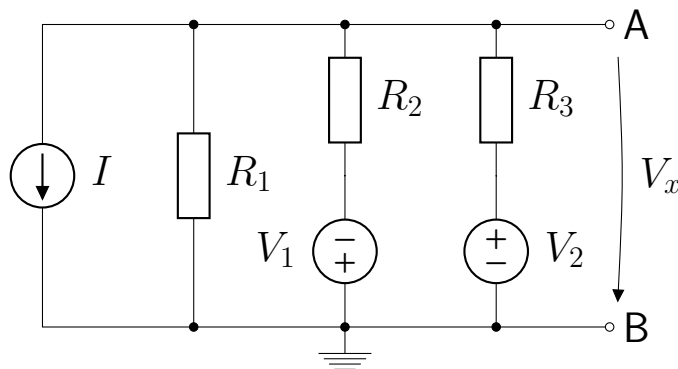


# Seminars - 4<sup>th</sup> week

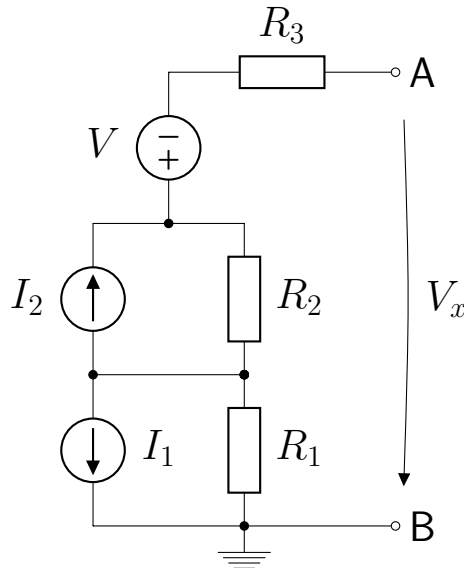
1. For the circuit in the figure below find voltage seen at terminals A-B,  $V_x$ .  $V_1 = 8\text{ V}$ ,  $V_2 = 12\text{ V}$ ,  $I = 8\text{ A}$ ,  $R_1 = 8\ \Omega$ ,  $R_2 = 1.6\ \Omega$ ,  $R_3 = 2\ \Omega$ .




2. For the circuit in the figure below find voltage seen at terminals A-B,  $V_x$ .  $V = 10\text{ V}$ ,  $I_1 = 2\text{ A}$ ,  $I_2 = 5\text{ A}$ ,  $R_1 = 8\ \Omega$ ,  $R_2 = 6\ \Omega$ ,  $R_3 = 10\ \Omega$ .



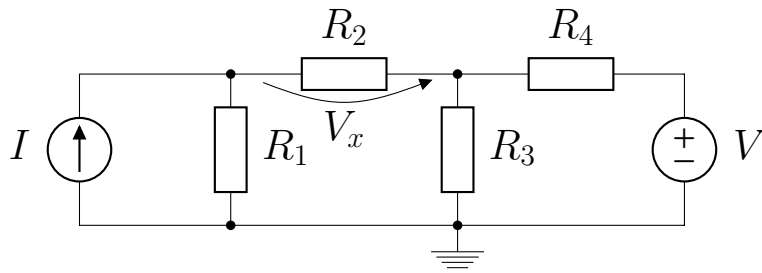
3. For the circuit in the figure below find voltage  $V_x$ .  $V = 60\text{ V}$ ,  $I = 0.2\text{ A}$ ,  $R_1 = 360\ \Omega$ ,  $R_2 = 400\ \Omega$ ,  $R_3 = 400\ \Omega$ ,  $R_4 = 600\ \Omega$ .



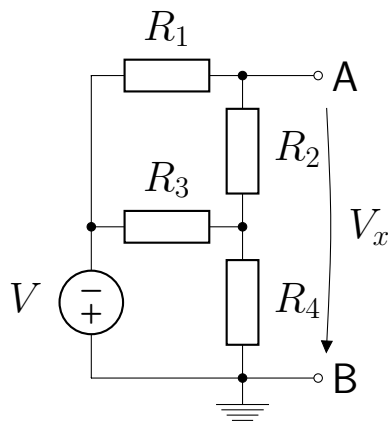4. For the circuit in the figure below find its Thevenin equivalent circuit seen at terminals A-B.  $V = 10\text{ V}$ ,  $R_1 = 1\text{ k}\Omega$ ,  $R_2 = 2\text{ k}\Omega$ ,  $R_3 = 2\text{ k}\Omega$ ,  $R_4 = 4\text{ k}\Omega$ .



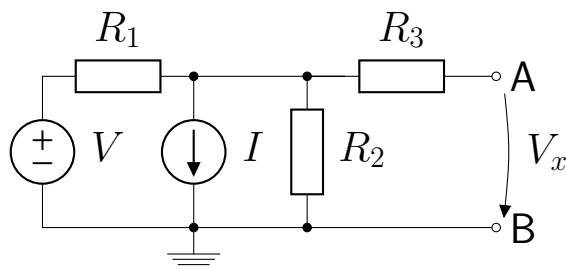5. For the circuit in the figure below find its Thevenin equivalent circuit seen at terminals A-B.  $V = 20\text{ V}$ ,  $I = 10\text{ mA}$ ,  $R_1 = 2\text{ k}\Omega$ ,  $R_2 = 8\text{ k}\Omega$ ,  $R_3 = 2.4\text{ k}\Omega$ .



6. For the circuit in the figure below calculate currents, delivered to the circuit by both voltage sources. Next, calculate the voltage  $V_x$ .

