


## HW - 02

Design PT1000 based thermometer containing the AD623 instrumentation amplifier. The operating temp is  $-50^{\circ}\text{C}$  to  $400^{\circ}\text{C}$ . The output voltage is  $0\text{mV}$  to  $2.5\text{V}$ . The supply voltage is  $5\text{V}$ .

- Find resistor value in the bridge
- Find amplifier gain to comply output voltage
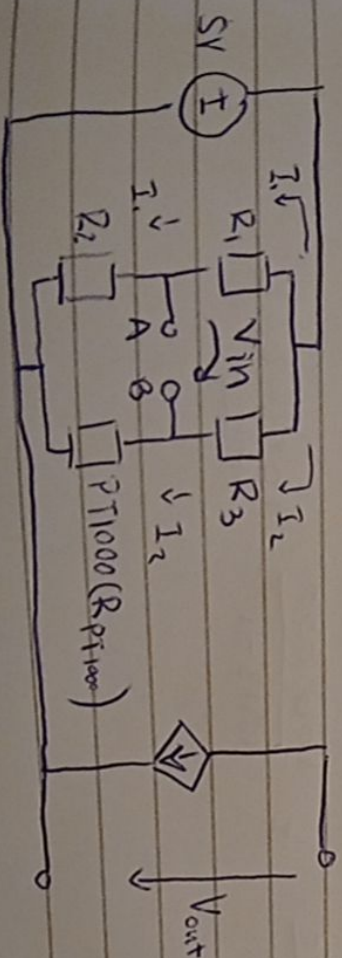
### Requirements

- Use AD623 datasheet to find value of gain control resistor (see datasheet for details)



$$V_{R_1} = V_{R_3}$$

$$V_{R_2} = V_{PT1000}$$

$$\frac{V_{R_1}}{V_{R_2}} = \frac{V_{R_3}}{V_{PT1000}}$$

$$\frac{I_1 R_1}{I_1 R_2} = \frac{I_2 R_3}{I_2 R_{PT1000}}$$

$$\frac{R_1}{R_2} = \frac{R_3}{R_{PT1000}} \quad (\text{cylindrical})$$

At  $-50^\circ\text{C}$ ,  $R_{PT1000} = 803.10 \Omega$

$V_{in} = 0$ , then  $R_{PT1000} = R_1 = R_2 = R_3$

Assume  $R_1 = R_2 = R_3 = 800 \Omega$ , ~~they're~~ the resistor values

$$V_A = V_{sup} \cdot \frac{R_{PT1000}}{R_{PT1000} + R_2} = 5 \cdot \frac{803.10}{803.10 + 800} = 2.505 \text{ V}$$

$$V_B = V_{sup} \cdot \frac{R_3}{R_1 + R_3} = 5 \cdot \frac{800}{800 + 800} = 2.5 \text{ V}$$

$$V_{in} = 2.505 - 2.5 = 0.005 \text{ V}$$

At  $400^\circ\text{C}$ ,  $R_{PT1000} = 2470.90 \Omega$

~~they're~~ ~~the resistor values~~

$$V_A = 5 \cdot \frac{2470.90}{2470.90 + 800} = 3.777 \text{ V}$$

$$V_B = 5 \cdot \frac{800}{800 + 800} = 2.5 \text{ V}$$

$$V_{in} = 3.777 - 2.5 = 1.277 \text{ V} \approx 1.3 \text{ V}$$

$V_{out} = 2.5 \text{ V}$  at  $400^\circ\text{C}$

$$\therefore G = \frac{V_{out}}{V_{in}} = \frac{2.5}{1.3} = 1.923$$

$$R_G = \frac{100\,000}{G-1} = \frac{100\,000}{1.923-1} = 108342 \Omega$$