
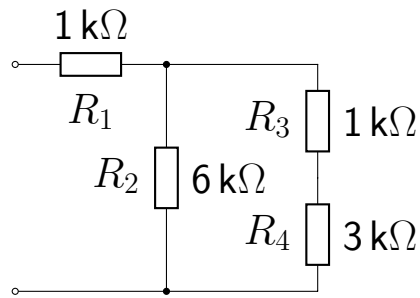


# Seminars - 2<sup>nd</sup> week

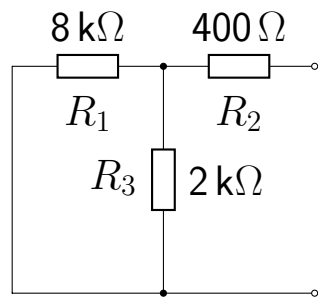
1. For the circuit in the figure below find total equivalent resistance  $R_{eq}$ .




2. For the circuit in the figure below find total equivalent resistance  $R_{eq}$ .



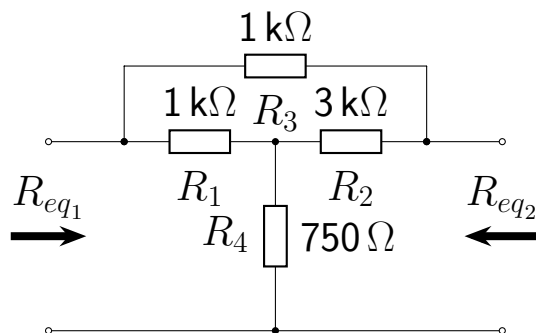
3. For the circuit in the figure below find total equivalent resistance  $R_{eq_1}$  for the left-handed pair of terminals, and  $R_{eq_2}$  for the right-handed pair of terminals.



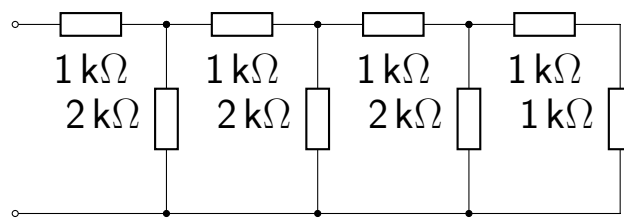
4. For the circuit in the figure below find total equivalent resistance  $R_{eq}$ .



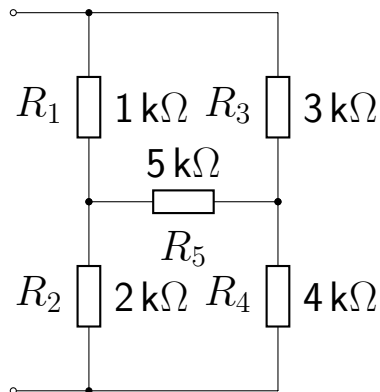
5. For the circuit in the figure below find total equivalent resistance  $R_{eq}$ .



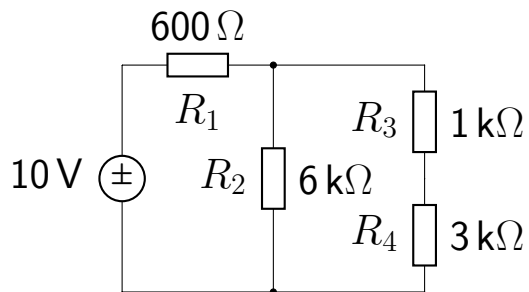
6. In the circuit in the figure below calculate all device voltages.



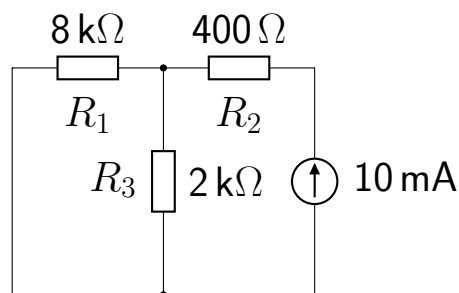
7. In the circuit in the figure below calculate all device voltages and currents.



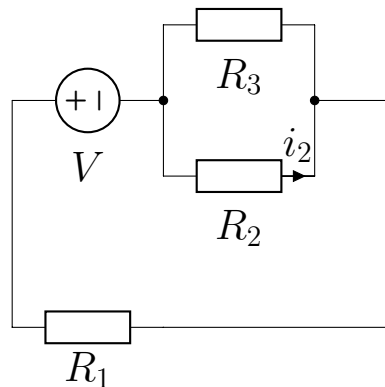8. In the circuit in the figure below calculate current  $i_2$ , if  $V = 11\text{V}$ ,  $R_1 = 1\Omega$ ,  $R_2 = 2\Omega$ ,  $R_3 = 3\Omega$ .



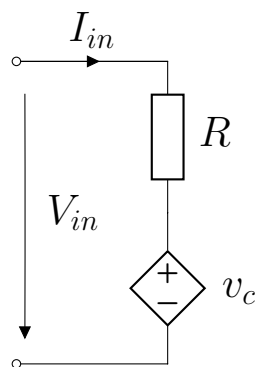9. For the circuit in the figure below find relationship between input voltage and input current (the input resistance of the circuit  $R_{in}$ ).  
 $v_c = AV_{in}$



10. In the circuit in the figure below are two batteries, represented by voltage sources  $V_1 = 1.5\text{V}$  and  $V_2 = 1.2\text{V}$  and resistors  $R_1 = 0.2\Omega$  and  $R_2 = 0.3\Omega$  connected in parallel. Find total voltage  $V_t$ .

